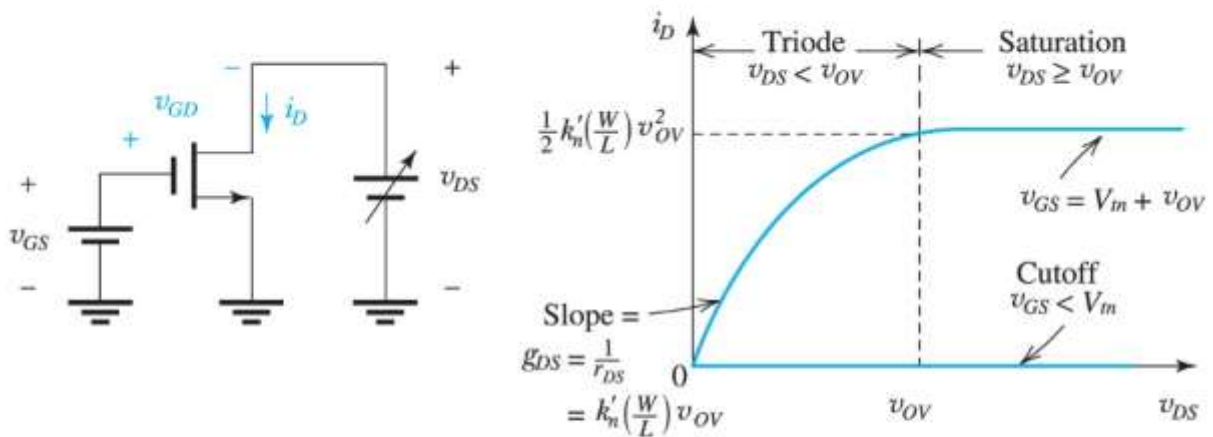


## NMOS Characteristics

**Table 5.1** Regions of Operation of the Enhancement NMOS Transistor



- $v_{GS} < V_{in}$ : no channel; transistor in cutoff;  $i_D = 0$
- $v_{GS} = V_{in} + v_{OV}$ : a channel is induced; transistor operates in the triode region or the saturation region depending on whether the channel is continuous or pinched off at the drain end;

### Triode Region

Continuous channel, obtained by:

$$v_{GD} > V_{in}$$

or equivalently:

$$v_{DS} < v_{OV}$$

Then,

$$i_D = k'_n \left( \frac{W}{L} \right) \left[ (v_{GS} - V_{in}) v_{DS} - \frac{1}{2} v_{DS}^2 \right]$$

or equivalently,

$$i_D = k'_n \left( \frac{W}{L} \right) \left( v_{OV} - \frac{1}{2} v_{DS} \right) v_{DS}$$

### Saturation Region

Pinched-off channel, obtained by:

$$v_{GD} \leq V_{in}$$

or equivalently:

$$v_{DS} \geq v_{OV}$$

Then


$$i_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) (v_{GS} - V_{in})^2$$

or equivalently,

$$i_D = \frac{1}{2} k'_n \left( \frac{W}{L} \right) v_{OV}^2$$

## PMOS Characteristics

**Table 5.2** Regions of Operation of the Enhancement PMOS Transistor

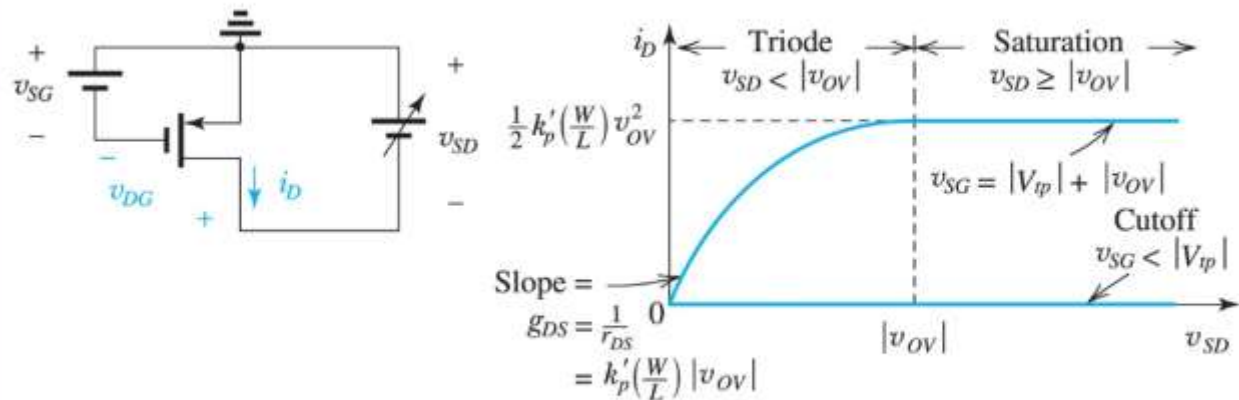

- $v_{SG} < |V_{tp}|$ : no channel; transistor in cutoff;  $i_D = 0$
- $v_{SG} = |V_{tp}| + |v_{OV}|$ : a channel is induced; transistor operates in the triode region or in the saturation region depending on whether the channel is continuous or pinched off at the drain end;

### Triode Region

Continuous channel, obtained by:

$$v_{DG} > |V_{tp}|$$

or equivalently

$$v_{SD} < |v_{OV}|$$

Then

$$i_D = k_p' \left( \frac{W}{L} \right) \left[ (v_{SG} - |V_{tp}|) v_{SD} - \frac{1}{2} v_{SD}^2 \right]$$

or equivalently

$$i_D = k_p' \left( \frac{W}{L} \right) \left( |v_{OV}| - \frac{1}{2} v_{SD} \right) v_{SD}$$

### Saturation Region

Pinched-off channel, obtained by:

$$v_{DG} \leq |V_{tp}|$$

or equivalently

$$v_{SD} \geq |v_{OV}|$$


Then

$$i_D = \frac{1}{2} k_p' \left( \frac{W}{L} \right) (v_{SG} - |V_{tp}|)^2$$

or equivalently

$$i_D = \frac{1}{2} k_p' \left( \frac{W}{L} \right) v_{OV}^2$$

## MOSFET Small Signal Characteristics

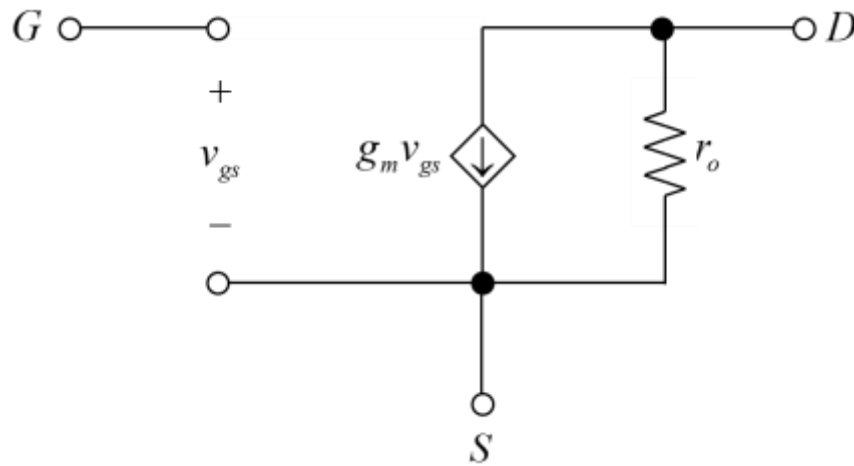

NMOS

$$g_m = \mu_n C_{ox} \left( \frac{W}{L} \right) V_{OV} = \sqrt{2 \mu_n C_{ox} \left( \frac{W}{L} \right) I_D} = \frac{2I_D}{V_{OV}}$$


$$r_o = V_A / I_D = 1 / \lambda I_D$$

PMOS

$$g_m = \mu_p C_{ox} \left( \frac{W}{L} \right) |V_{OV}| = \sqrt{2 \mu_p C_{ox} \left( \frac{W}{L} \right) I_D} = \frac{2I_D}{|V_{OV}|}$$

$$r_o = |V_A| / I_D = 1 / |\lambda| I_D$$
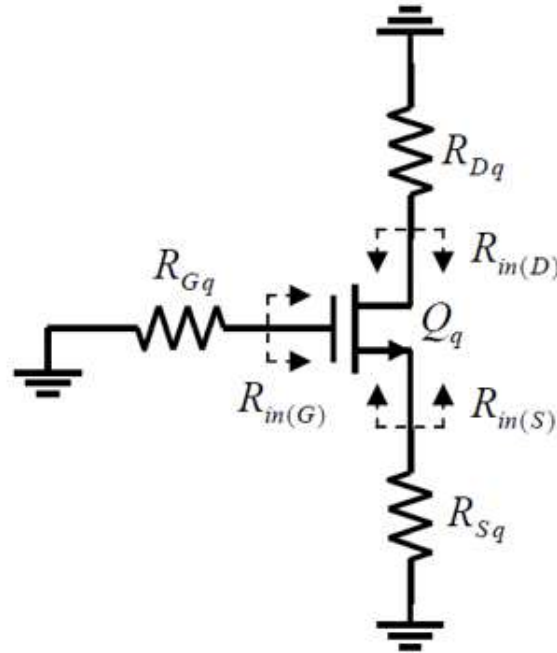
## MOSFET Small Signal Equivalent Resistance



$$R_{in(G)} = \infty \quad G_{in(G)} = 0$$


$$R_{in(D)} = \frac{g_{mq} + g_{oq} + G_{Sq}}{g_{oq} G_{Sq}} \quad G_{in(D)} = \frac{g_{oq} G_{Sq}}{g_{mq} + g_{oq} + G_{Sq}}$$

$$R_{in(S)} = \frac{g_{oq} + G_{Dq}}{G_{Dq} (g_{mq} + g_{oq})} \quad G_{in(S)} = \frac{G_{Dq} (g_{mq} + g_{oq})}{g_{oq} + G_{Dq}}$$

---

## MOSFET Common Source Amplifier w/o Source Resistor

---

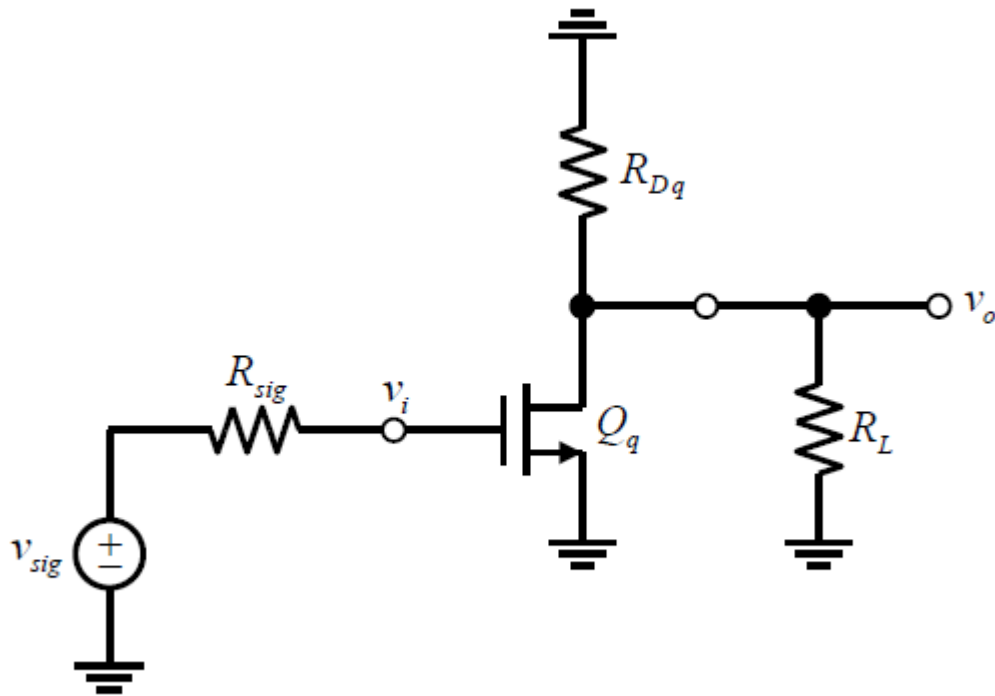


$$R_{in} = \infty \quad G_{in} = 0$$

$$G_o = g_{oq} + G_{Dq} \quad R_o = r_{oq} \parallel R_{Dq}$$

$$G_m = -g_{mq}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$
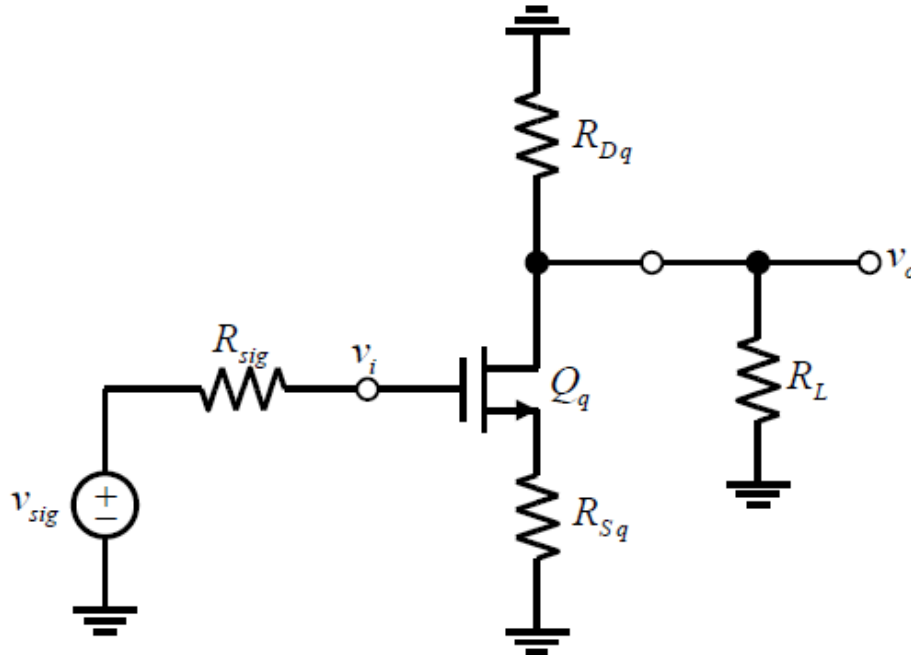
## MOSFET Common Source Amplifier w/ Source Resistor



$$R_{in} = \infty \quad G_{in} = 0$$

$$G_o = G_o' + G_{Dq} \quad R_o = R_o' \parallel R_{Dq}$$

$$G_o' = \frac{g_{oq} G_{Sq}}{g_{mq} + g_{oq} + G_{Sq}} \quad R_o' = R_{Sq} + r_{oq} + g_{mq} r_{oq} R_{Sq}$$


$$G_m = -\frac{g_{mq} G_{Sq}}{g_{mq} + g_{oq} + G_{Sq}}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$

---

## MOSFET Common Drain Amplifier w/o Drain Resistor

---

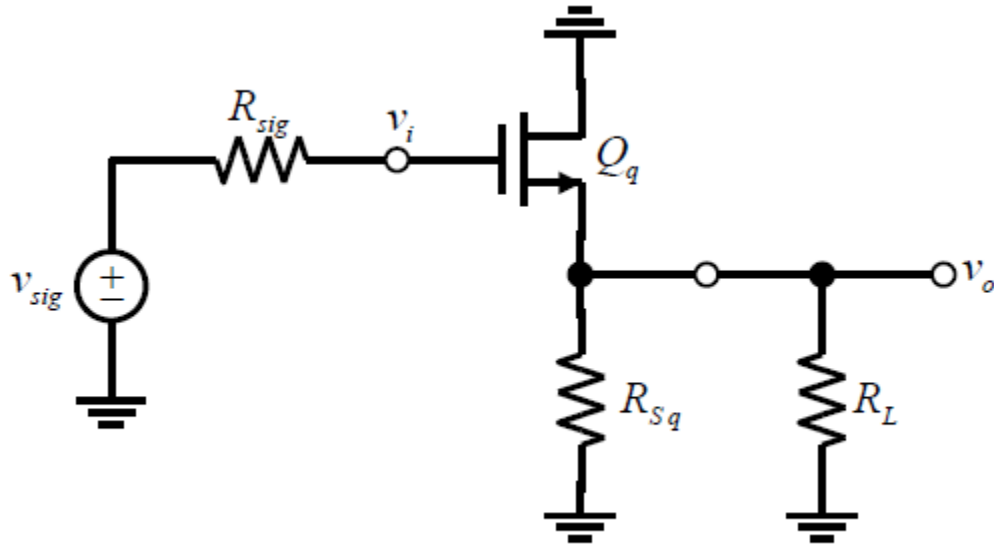


$$R_{in} = \infty \quad G_{in} = 0$$

$$G_o = g_{mq} + g_{oq} + G_{Sq} \quad R_o = (1/g_{mq}) \parallel r_{oq} \parallel R_{Sq}$$

$$G_m = g_{mq}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$
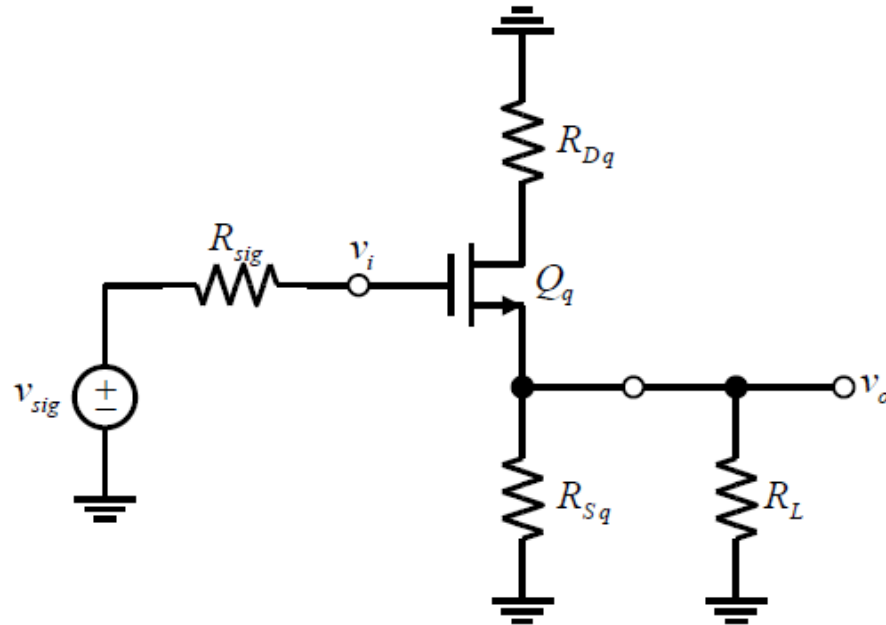
## MOSFET Common Drain Amplifier w/ Drain Resistor



$$R_{in} = \infty \quad G_{in} = 0$$

$$G_o = G_o' + G_{Sq} \quad R_o = R_o' \parallel R_{Sq}$$


$$G_o' = \frac{G_{Dq} (g_{mq} + g_{oq})}{g_{oq} + G_{Dq}} \quad R_o' = \frac{g_{oq} + G_{Dq}}{G_{Dq} (g_{mq} + g_{oq})}$$

$$G_m = \frac{g_{mq} G_{Dq}}{g_{oq} + G_{Dq}}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$



## MOSFET Common Gate Amplifier

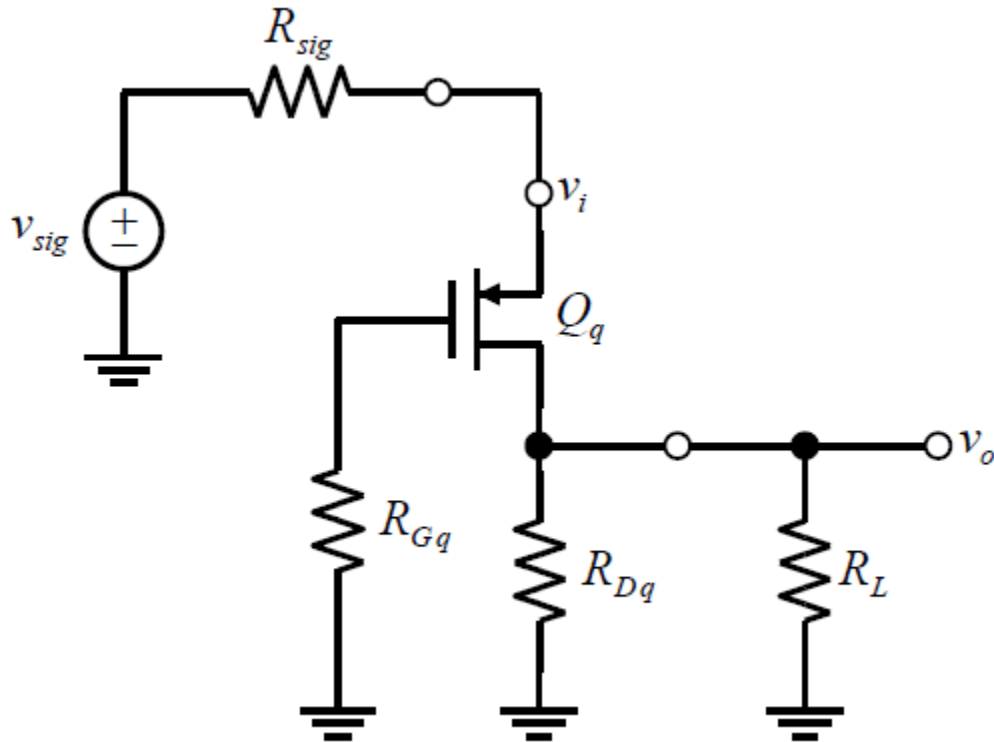


$$R_{in} = \frac{g_{oq} + G_{Dq} + G_L}{(g_{mq} + g_{oq})(G_{Dq} + G_L)} \quad G_{in} = \frac{(g_{mq} + g_{oq})(G_{Dq} + G_L)}{g_{oq} + G_{Dq} + G_L}$$

$$G_o = g_{oq} + G_{Dq} \quad R_o = r_{oq} \parallel R_{Dq}$$

$$G_m = g_{mq} + g_{oq}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$

## MOSFET Differential Amplifier

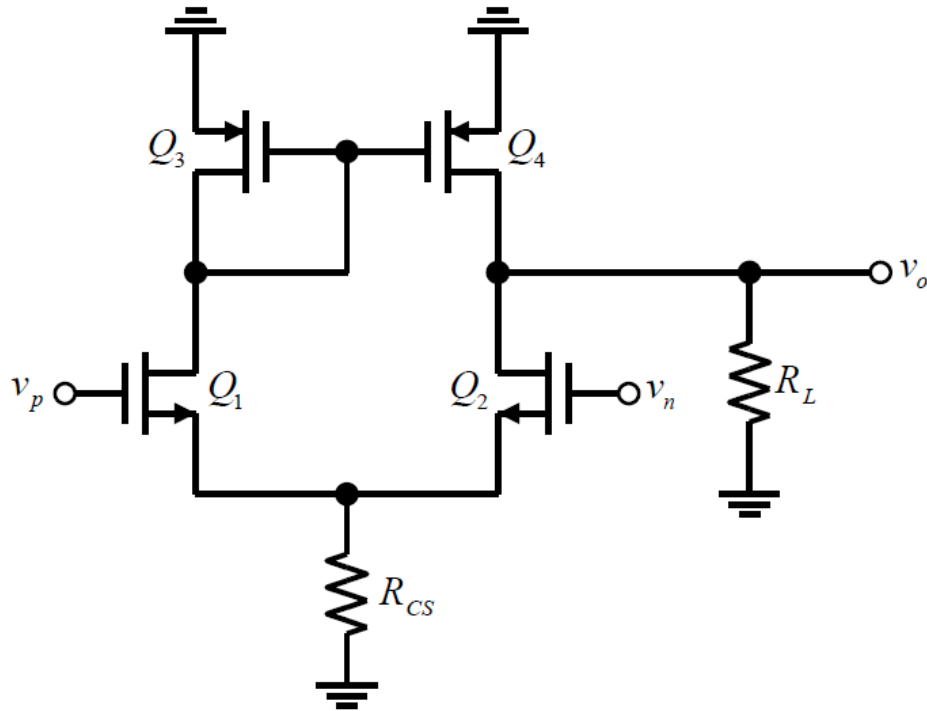

$$R_{in} = \infty \quad G_{in} = 0$$

$$G_o = Xg_{o2} + g_{o4} \quad R_o = \frac{1}{Xg_{o2} + g_{o4}}$$

$$G_m = Xg_{m2}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$

$$X = \frac{1}{2} \left[ 1 + \frac{(W/L)_4}{(W/L)_3} \right]$$

---

## BJT Equations in Active Mode

---

*npn*

$$v_{BE} = 0.7 \text{ V}$$

$$v_{CE} \geq V_{CE(\text{SAT})} = 0.3\text{V}$$

$$i_C = I_S e^{v_{BE}/V_T}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

$$i_C = \beta i_B$$

$$i_E = (\beta + 1) i_B$$

*pnp*

$$v_{EB} = 0.7 \text{ V}$$

$$v_{EC} \geq V_{EC(\text{SAT})} = 0.3\text{V}$$

$$i_C = I_S e^{v_{EB}/V_T}$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$i_C = \alpha i_E$$

$$i_E = i_C / \alpha$$

---

## BJT Equations in Saturation Mode

---

*npn*

$$v_{BE} = 0.7 \text{ V}$$

$$v_{CE} \cong V_{CE(\text{SAT})} = 0.2\text{V}$$

$$I_{C(\text{SAT})} = \beta_{\text{Forced}} I_B$$


$$\beta_{\text{Forced}} \leq \beta$$

*pnp*

$$v_{EB} = 0.7 \text{ V}$$

$$v_{EC} \cong V_{EC(\text{SAT})} = 0.2\text{V}$$


## BJT Small Signal Characteristics

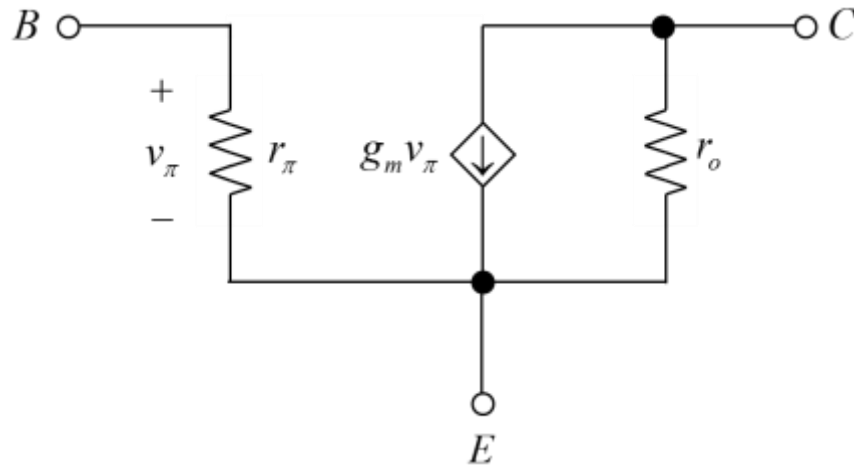

NPN & PNP

$$g_m = \frac{I_C}{V_T} \quad r_o = \frac{|V_A|}{I_C} \quad r_\pi = \frac{V_T}{I_B}$$
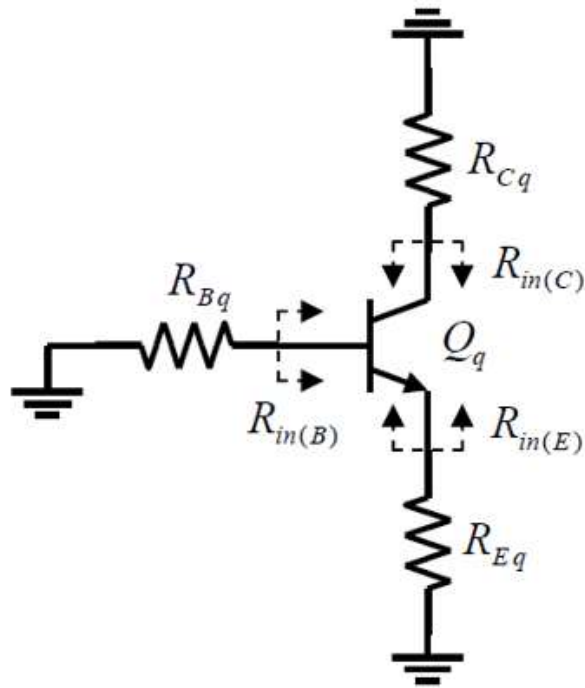
## BJT Small Signal Equivalent Resistance




$$R'_{in} = \frac{G_{Cq} + g_{oq} + G_{Cq} g_{mq} r_{\pi q}}{G_{Eq} G_{Cq} + G_{Eq} g_{oq} + G_{Cq} g_{oq}} \rightarrow R_{in(B)} = R'_{in} + r_{\pi q}$$

$$R_{in(E)} = \frac{R_x g_{oq} + R_x G_{Cq}}{G_{Cq} + g_{oq} + G_{Cq} g_{oq} R_x + G_{Cq} g_{mq} r_{\pi q}} \quad R_x = R_{Bq} + r_{\pi q}$$

$$R_{in(C)} = \frac{1 + G_{Eq} R_x + g_{oq} R_x + g_{mq} r_{\pi q}}{g_{oq} (1 + G_{Eq} R_x)} \quad R_x = R_{Bq} + r_{\pi q}$$
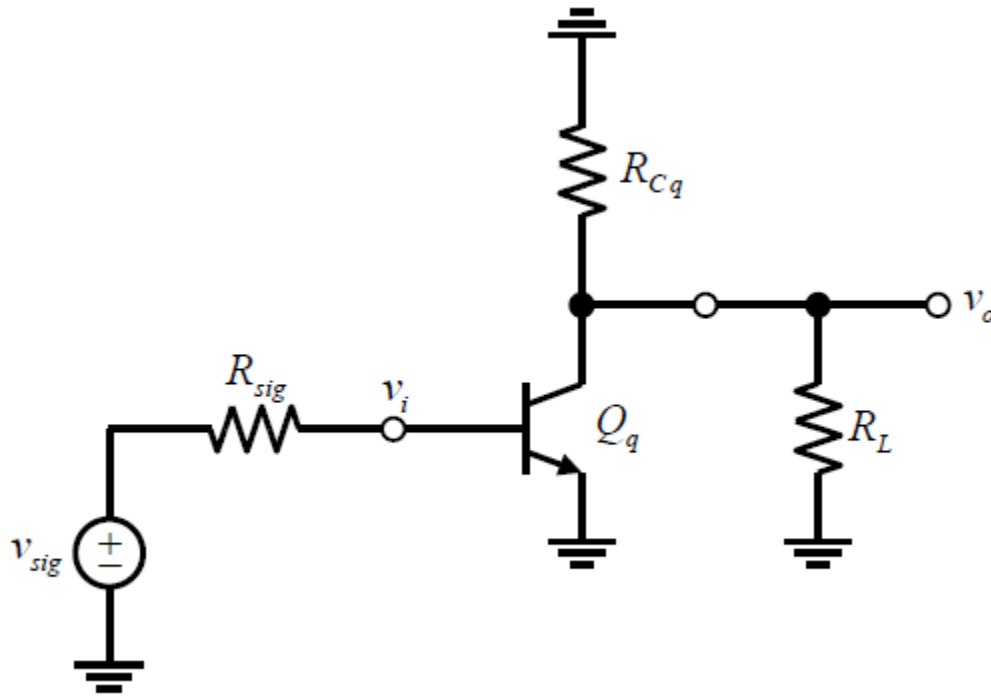
## BJT Common Emitter Amplifier w/o Emitter Resistor




$$R_{in} = r_{\pi q} \quad G_{in} = g_{\pi q}$$

$$G_o = g_{oq} + G_{Cq} \quad R_o = r_{oq} \parallel R_{Cq}$$

$$G_m = -g_{mq}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$
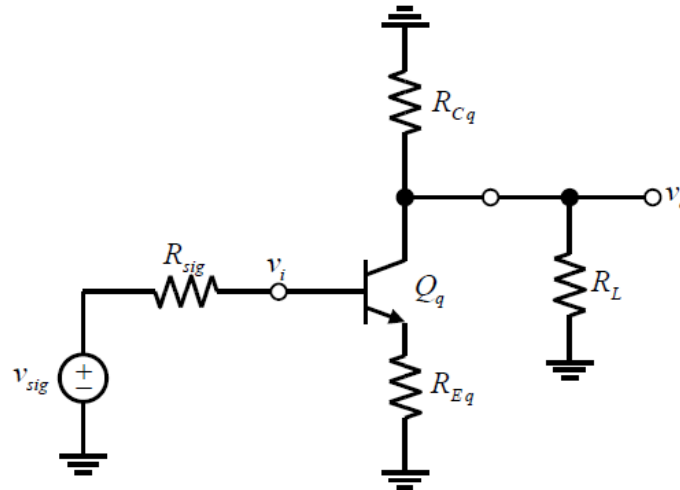
## BJT Common Emitter Amplifier w/ Emitter Resistor



$$R_{in} = r_{\pi q} + R'_{in} \quad G_{in} = \frac{g_{\pi} G'_{in}}{g_{\pi} + G'_{in}}$$

$$G'_{in} = \frac{(G'_{Cq} + G_{Eq}) g_{oq} + G'_C G_{Eq}}{g_{oq} + (\beta_q + 1) G'_C} \quad G'_C = G_{Cq} + G_L$$

$$G_o = G'_o + G_{Cq} \quad R_o = R'_o \parallel R_{Cq}$$


$$G'_o = \frac{g_{oq} G_{xq}}{g_{mq} + g_{oq} + G_{xq}} \quad R'_o = R_{xq} + r_{oq} + g_{mq} r_{oq} R_{xq}$$

$$G_{xq} = g_{\pi q} + G_{Eq}$$

$$G_m = \frac{g_{\pi q} g_{oq} - g_{mq} G_{Eq}}{g_{mq} + g_{oq} + G_{Eq}}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$
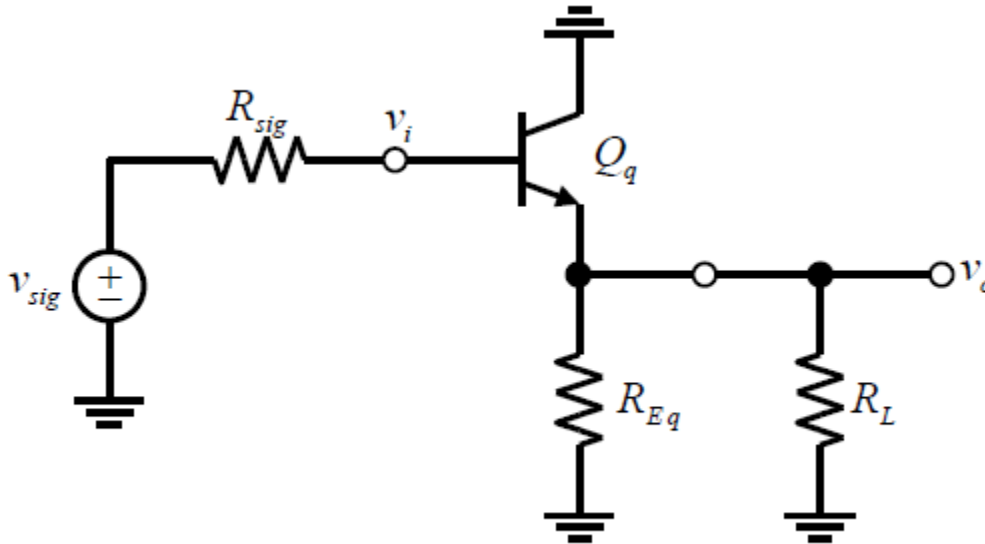
## BJT Common Collector Amplifier w/o Collector Resistor



$$R_{in} = r_{\pi q} + R'_{in} \quad G_{in} = \frac{g_{\pi} G'_{in}}{g_{\pi} + G'_{in}}$$

$$G'_{in} = \frac{g_{oq} + G'_{Eq}}{(\beta_q + 1)} \quad G'_{Eq} = G_{Eq} + G_L$$

$$G_o = G'_o + G_{Eq} \quad R_o = R'_o \parallel R_{Eq}$$


$$G'_o = g_{mq} + g_{\pi q} + g_{oq}$$

$$G_m = g_{mq} + g_{oq}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$


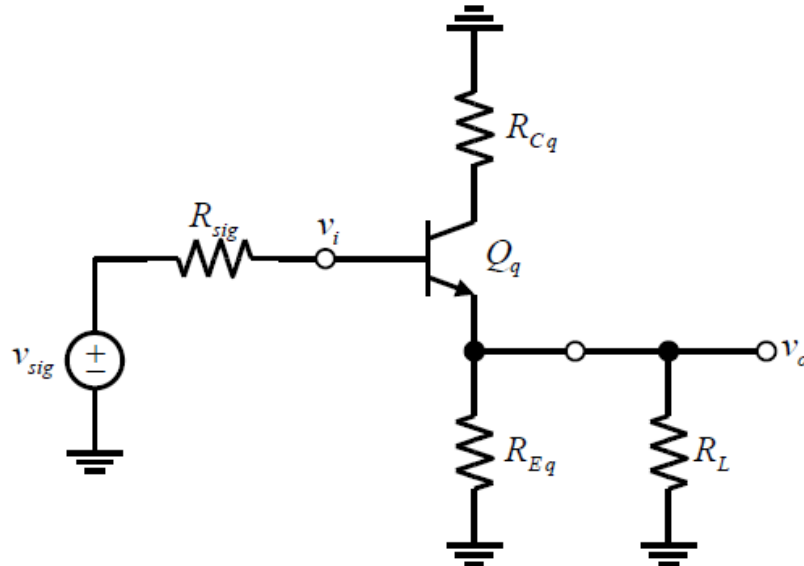
## BJT Common Collector Amplifier w/ Collector Resistor



$$R_{in} = r_{\pi q} + R'_{in} \quad G_{in} = \frac{g_{\pi} G'_{in}}{g_{\pi} + G'_{in}}$$

$$G'_{in} = \frac{(G'_{Eq} + G_{Cq}) g_{oq} + G_C G'_{Eq}}{g_{oq} + (\beta_q + 1) G_C} \quad G'_{Eq} = G_{Eq} + G_L$$


$$G_o = G'_o + G_{Eq} \quad R_o = R'_o \parallel R_{Eq}$$

$$G'_o = g_{\pi} + \frac{(g_{mq} + g_{oq}) G_{Cq}}{g_{oq} + G_{Cq}}$$

$$G_m = \frac{g_{mq} G_{Cq} + g_{\pi q} (g_{oq} + G_{Cq})}{g_{oq} + G_{Cq}}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$
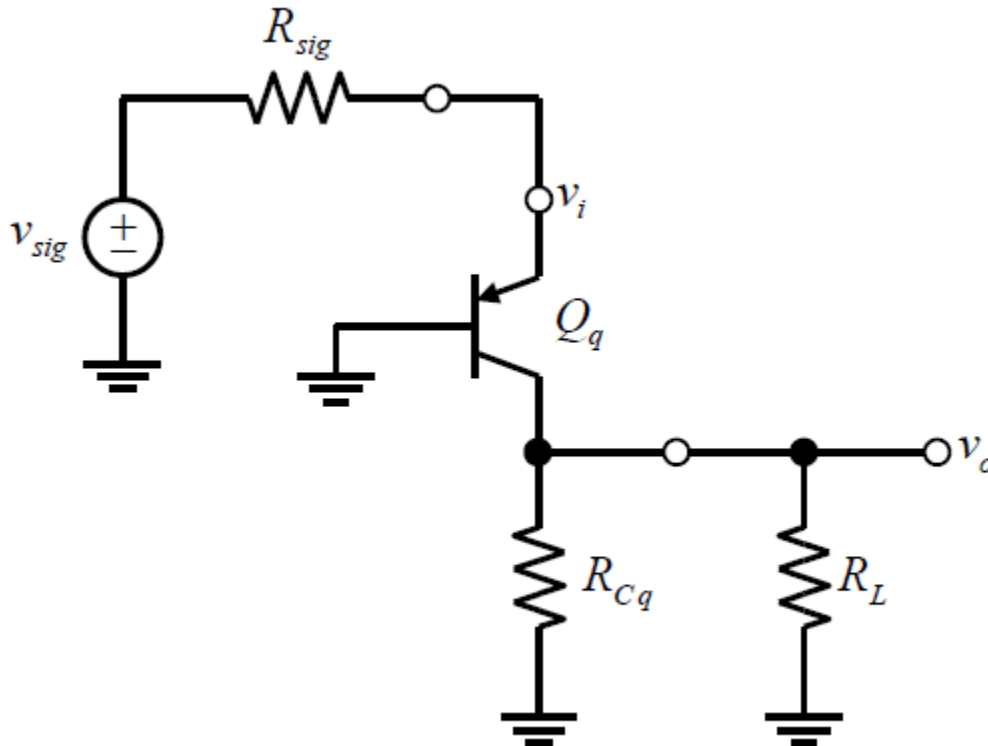
## BJT Common Base Amplifier w/o Base Resistor



$$R_{in} = r_{\pi q} + R'_{in} \quad G_{in} = \frac{g_{\pi} G'_{in}}{g_{\pi} + G'_{in}}$$


$$G'_{in} = \frac{(g_{mq} + g_{oq})(G_{Cq} + G_L)}{g_{oq} + G_{Cq} + G_L}$$

$$G_o = g_{oq} + G_{Cq} \quad R_o = r_{oq} \parallel R_{Cq}$$

$$G_m = g_{mq} + g_{oq}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$
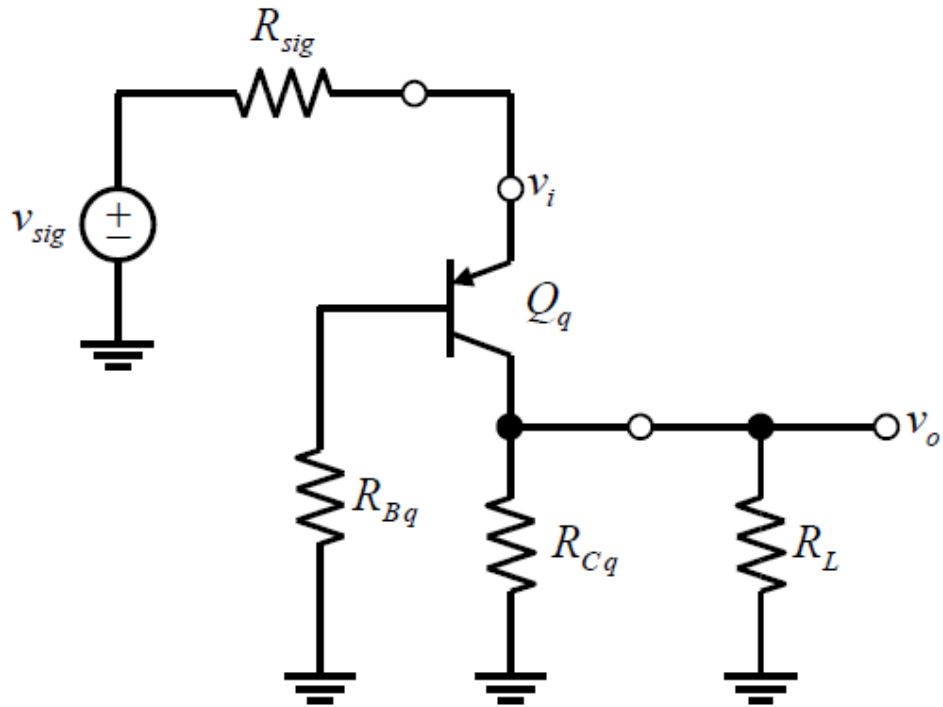
## BJT Common Base Amplifier w/ Base Resistor



$$R_{in} = r_{\pi q}' \parallel R_{in}' \quad G_{in} = g_{\pi}' + G_{in}'$$


$$G_{in}' = \frac{(g_{mq}' + g_{oq})(G_{Cq} + G_L)}{g_{oq} + G_{Cq} + G_L} \quad g_{\pi q}' = \frac{g_{\pi} G_{Bq}}{g_{\pi q} + G_{Bq}} \quad g_{mq}' = \frac{g_{\pi q}' g_{mq}}{g_{\pi q}}$$

$$G_o = g_{oq} + G_{Cq} \quad R_o = r_{oq}' \parallel R_{Cq}$$

$$G_m = g_{mq}' + g_{oq}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$

## BJT Differential Amplifier

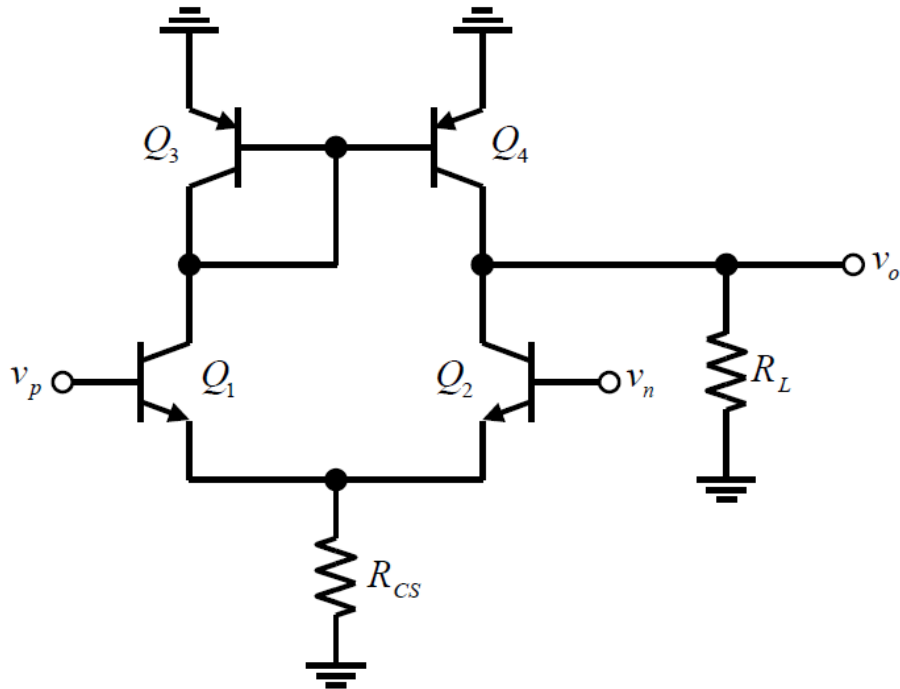

$$R_{in} = 2r_{\pi 2} \quad G_{in} = g_{\pi} / 2$$

$$G_o = Xg_{o2} + g_{o4} \quad R_o = \frac{1}{Xg_{o2} + g_{o4}}$$

$$G_m = Xg_{m2}$$

$$A_{vo} = G_m R_o \quad A_v = \frac{G_m}{G_o + G_L}$$

$$X = \frac{1}{2} \left[ 1 + \frac{A_{E4}}{A_{E3}} \right]$$